


MAE 140: Linear Circuits – Winter 2013

Circuit Demonstration #3


# Audio Mixer




# What is an audio mixer?

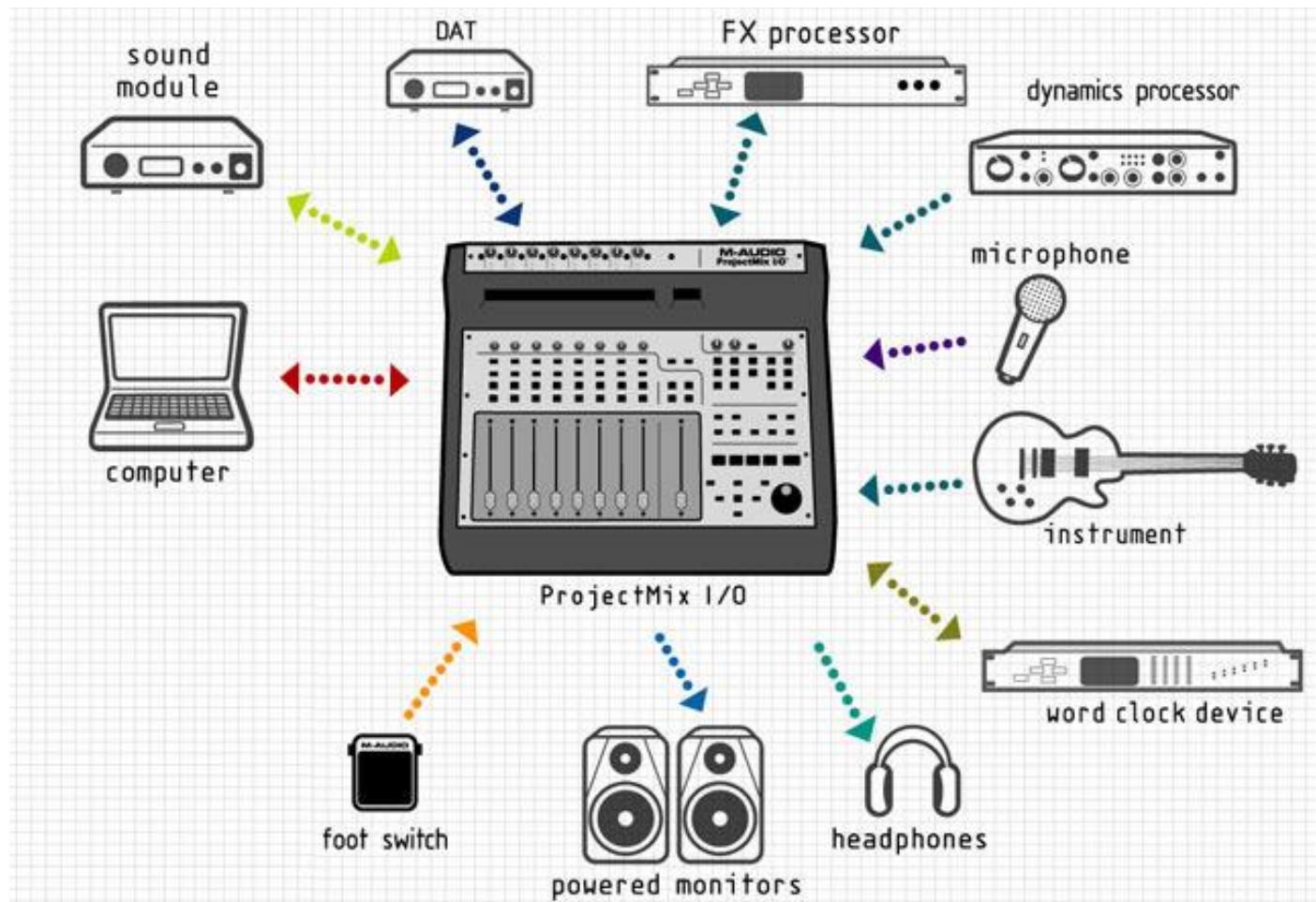

## 2-channel audio mixer using LM324

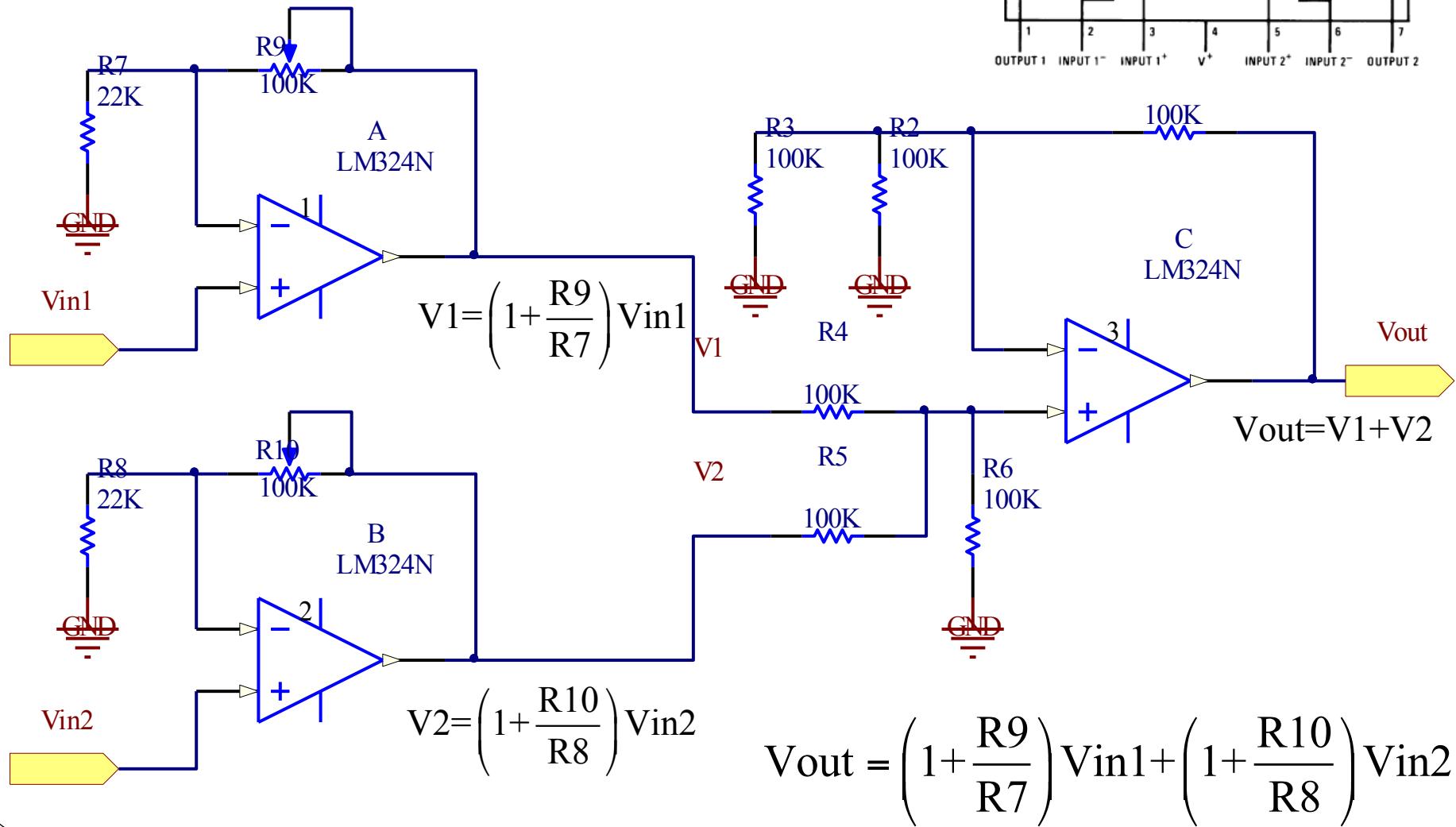

# Circuit close-up

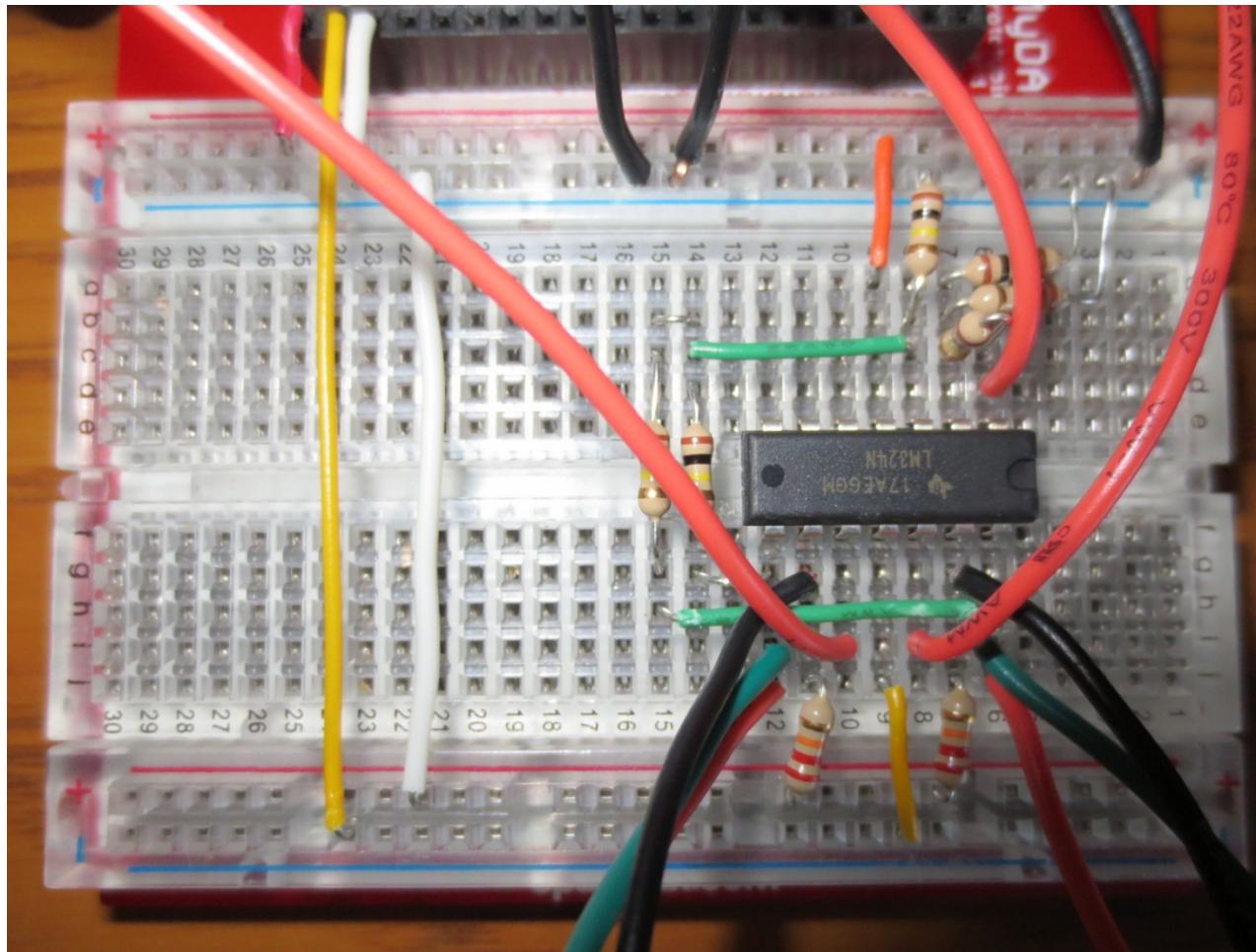

# Experiment Setup

